```
1/0 and state Models
            Ex1: Voltage control of RLC circuit
                                                         U = Source voltage (input) → variable used to control (offset) system
                        y=voltage across C (output) -> variable to measure and for control
                      kvL: Ri+L. di +y-u=0
                      KCL: i = C dy (2) t is time
                      Eliminate i to get I/O model between u & y
                       Take \frac{d}{dt} in (2) and sub-in (1): LC \frac{d^2y}{dt^2} + RC \frac{dy}{dt} + y=u (3) \rightarrow 1/0 model for RLC circuit
                         2nd order ODE, linear, const. coeff.
                       To solve it, we need 2 I.C. y(0) & \dot{y}(0), where \dot{y} = \frac{dy}{dt}
                      >Get a State (space) Model by introducing auxiliary variables to covert from
                        a 2nd order ODE - a set of 2 1st order ODE
                        Let { X1 = y (= voltage across C) generalizable to any RLC circuit 
 X2 = i (= current through L) = C dy
                         and x = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} \in \mathbb{R}^2, state vector X(0) = \begin{bmatrix} x_1(0) \\ x_2(0) \end{bmatrix} = \begin{bmatrix} y(0) \\ y(0) \end{bmatrix}
                                                   \frac{dx_1}{dt} \stackrel{\textcircled{\scriptsize d}}{=} \frac{dy}{dt} \stackrel{\text{KCL}}{=} \frac{1}{c} \cdot i \stackrel{\textcircled{\scriptsize d}}{=} \frac{1}{c} x_2
                                                  \frac{dx_s}{dt} = \frac{di}{dt} \frac{kcL}{=} c \cdot \frac{d^3y}{dt^2} = -\frac{R}{L} c \frac{dy}{dt} - \frac{1}{L}y + \frac{1}{L}y
                                                                                                                            X(0) = [x,(0)]
Overall State-model

\bigoplus_{\substack{\dot{x}_1 = \dot{c} \\ \dot{x}_2 = -\dot{c} \\ \dot{x}_1 = \dot{c} \\ \dot{x}_2 = -\dot{c} \\ \dot{x}_1 = \dot{c} \\ \dot{x}_2 = -\dot{c} \\ \dot{x}_1 = \dot{c} \\ \dot{x}_2 = \dot{c} \\ \dot{x}_2 = \dot{c} \\ \dot{x}_2 = \dot{c} \\ \dot{x}_1 = \dot{c} \\ \dot{x}_2 = \dot{c} \\ \dot{x}_2 = \dot{c} \\ \dot{x}_1 = \dot{c} \\ \dot{x}_2 = \dot{c} \\ \dot{x}_3 = \dot{c} \\ \dot{x
                             \begin{cases} \dot{x} = Ax + Bu & \text{where } D = 0 \\ y = Cx + Du & \text{general state model (matrix form)} \end{cases} 
                      E.g 3 capacitors, 2 inductors $ 5 state variables, 5 1st ode, x ER, A is 5 x 5
```